

# Pre-lab - Exp - 7 :

Name - Balasubramaniam MC

Rolls - EE18B155

①  $R'$  of Adder can be any value - in this case, taken  $1k = R$   
We know that  $V_{inac}$  - has 2x amplitude of  $V_{in1}$

$$V_{in1 \text{ amp}} = 0.45V \quad \text{or } (0.45V_{rms})$$

$$\therefore V_{inac \text{ amp}} = \underline{0.90V}$$

$\therefore$  The peak detector detects peak of 0 biased, 0.9V rms.  
Sine wave i/p of 0.9V  $= V_{peak}$

$$V_{ref} = 250mV = \frac{(V_{peak}) \cdot R_3}{R_2 + R_3}$$


$$\therefore \frac{R_3}{R_2 + R_3} (\cancel{1.8}) = 0.25V$$

$$\therefore \cancel{1.8} R_3 = 0.25 R_2$$

$$\boxed{6.2 R_3 = R_2} \quad \cancel{1.3 R_3 = 5 R_2}$$

$$\text{or } \boxed{R_3 = 0.16 R_2}$$

$$V_{\text{peak ripple}} = 100mV.$$

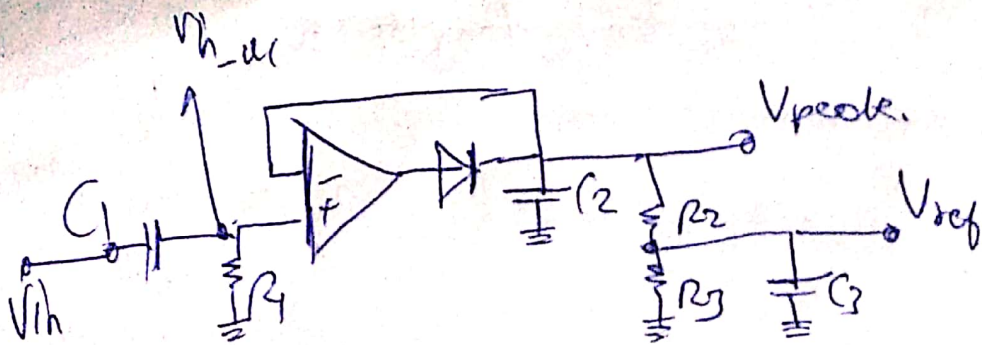


$V_{in\_ac}$

$V_{in1}, V_{in2}$  max amp. =  $0.75V$  ( $V_m=1$ ) Then, max amp. at

$$V_{in\_ac} = 0.90V \text{ (since it's a BPF)}$$

$V_{peak\_ripple} = 100mV$   
max.


For ripple at  $V_{peak}$ :-

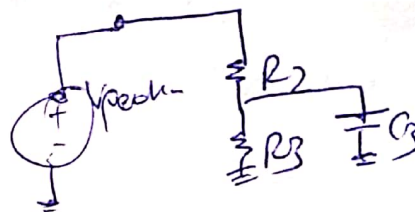

is the circuit,

RC const.  $\therefore R_{eff} = \frac{R_2 R_3}{R_2 + R_3}$  ( $C_{off} = C_3$ )
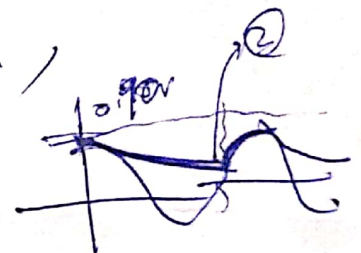
$$(0.90V) \cdot \cos(2\pi \cdot f \cdot t) = 0.90 \left( \frac{1}{2} e^{-t/RC} \right)$$



at (2),  $(0.90V) - 100mV = 0.90 e^{-\frac{1}{RC}}$  Discharge =  $\frac{1}{6}$

$$+ \ln\left(\frac{0.90}{0.80}\right) \cdot t = 1/RC$$

$$RC = \frac{1}{f \ln\left(\frac{0.90}{0.80}\right)} = \frac{8.49}{f}$$

We know  $R_3 = 0.16 R_2$

$$\frac{(0.16) R_2 \cdot C_3}{1.16} = \frac{8.49}{f}$$

$$\therefore R_2 C_3 = 61.55ms$$

Take  $f = 1kHz$ , so that for higher freq Exp 1 will be lesser.

Let's take  $R_2 = 1k$ ,  $C_3 = 61.55\mu F$ , the ripple was found to be less than 100mV range; and  $V_{ripple}$  for  $V_{ref}$  was  $< 10mV$ . This works for both,  $3kHz$  and  $1kHz$ .

$$\therefore R = 1k, R_2 = 1k, R_3 = 160\Omega, C_3 = 61.55\mu F, C_2 = 5\mu$$

Finally, for the given BPF, we needed  $V_{ref}$  to hit 250mV.  $\therefore R_3$  had to be changed to  $1.27k$  to get 250mV. Other conditions still hold.



